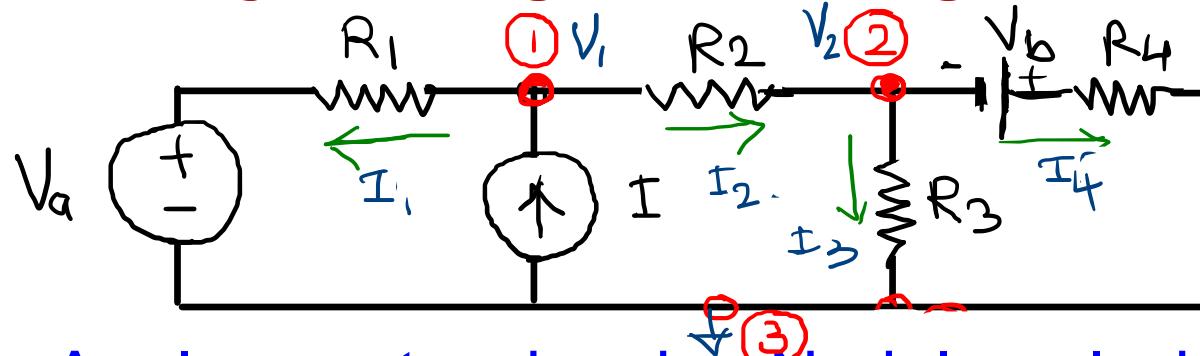


Network Analysis using Node Voltage Method (Nodal Analysis)



Steps to Analyze network using Nodal analysis:

1. Identify non-reference and a reference(datum) node. Mark node voltages.

→ Node ①, ② are Non-reference Nodes & node ③ is reference node

→ Node voltages V_1 & V_2 are assumed to be positive with respect to reference node ③

2. Write KCL at all Non-reference nodes.

$$\rightarrow \text{KCL at node } ①: I_1 + I_2 = I \quad \& \text{ KCL at node } ②: I_2 = I_3 + I_4$$

OR in terms of node voltages


$$\text{at node } ①: \frac{V_1 - V_a}{R_1} + \frac{V_1 - V_2}{R_2} = I \quad \dots \quad ① \quad \& \quad \frac{V_1 - V_2}{R_2} - \frac{V_2}{R_3} - \left(\frac{V_2 + V_b}{R_4} \right) = 0$$

3. Solve the node voltage equations simultaneously to find every node voltage. (V_1 & V_2)

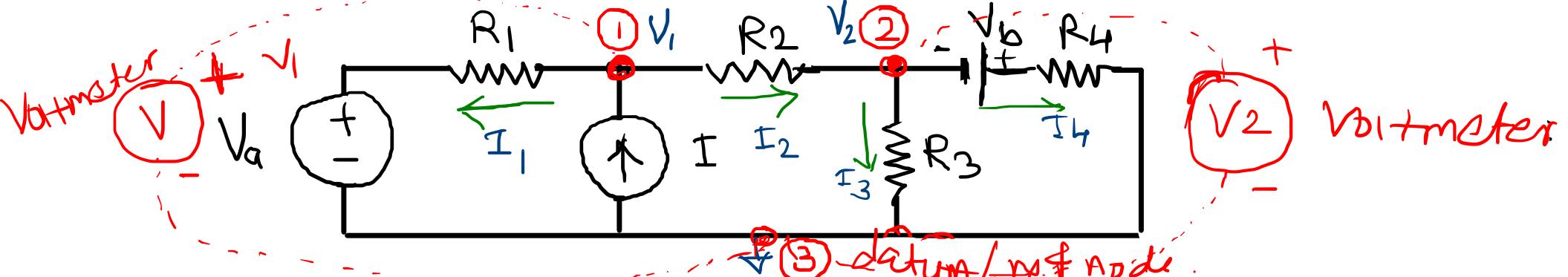4. Use node voltage to find current/voltage in any branch of the network.

$$\text{e.g. } V_{R_2} = V_1 - V_2, \quad I_{4n} = \frac{V_2 + V_b}{R_4} \quad \text{etc.}$$

Network Analysis using Node Voltage Method (Nodal Analysis)




Steps to Analyze network using Nodal analysis:

1. Identify non-reference and a reference(datum) node. Mark node voltages.

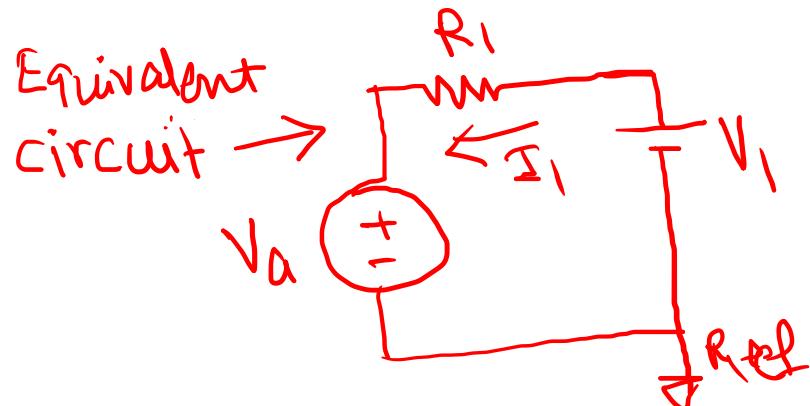2. Write KCL at all Non-reference nodes.

KCL at node ① $I_1 + I_2 = I$ & KCL at node ② $I_2 = I_3 + I_4$

To I_1 , I_2 , I_3 & I_4 in terms of V_1 & V_2




KVL to loop

$$-I_1 R_1 - V_a + V_1 = 0$$

$$I_1 = \frac{V_1 - V_a}{R_1}$$

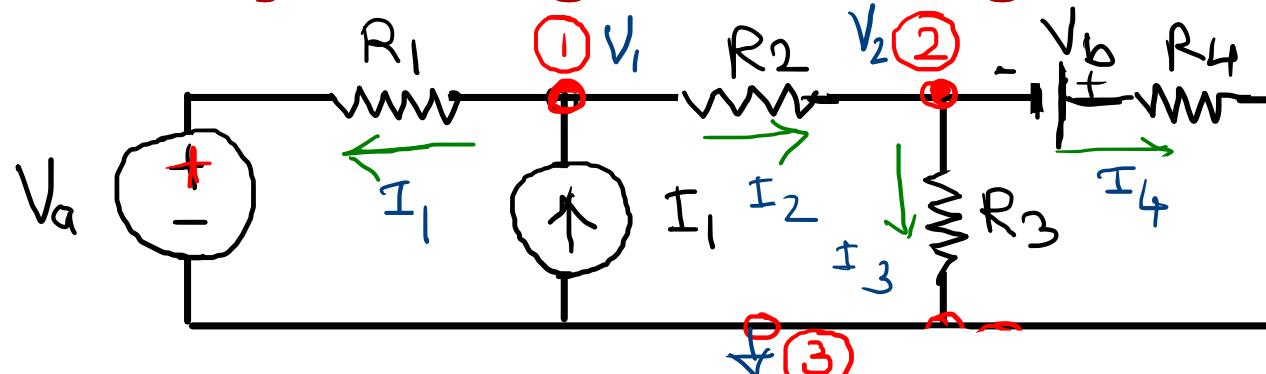Network Analysis using Node Voltage Method (Nodal Analysis)




$$I_1 = \frac{V_1 - V_a}{R_1}$$

Steps to Analyze network using Nodal analysis:

1. Identify non-reference and a reference(datum) node. Mark node voltages.


2. Write KCL at all Non-reference nodes.

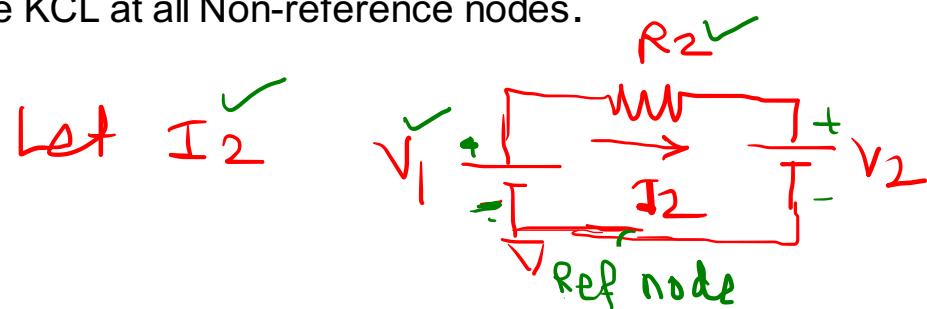


By KVL

$$V_1 - I_2 R_2 - V_2 = 0$$

$$I_2 = \frac{V_1 - V_2}{R_2}$$

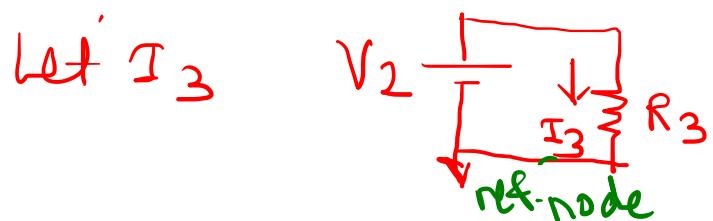

$$I_3 = \frac{V_2}{R_3}$$

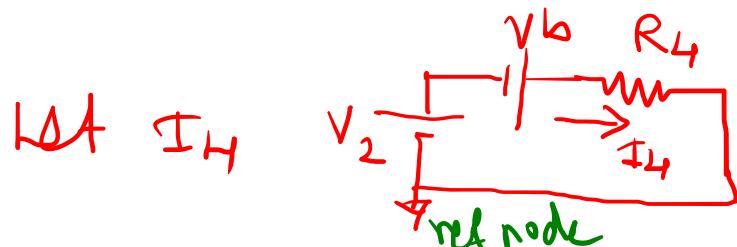

KVL



$$V_2 + V_b - I_4 R_4 = 0 \text{ so}$$

$$I_4 = \frac{V_2 + V_b}{R_4}$$

Network Analysis using nodal analysis

-1

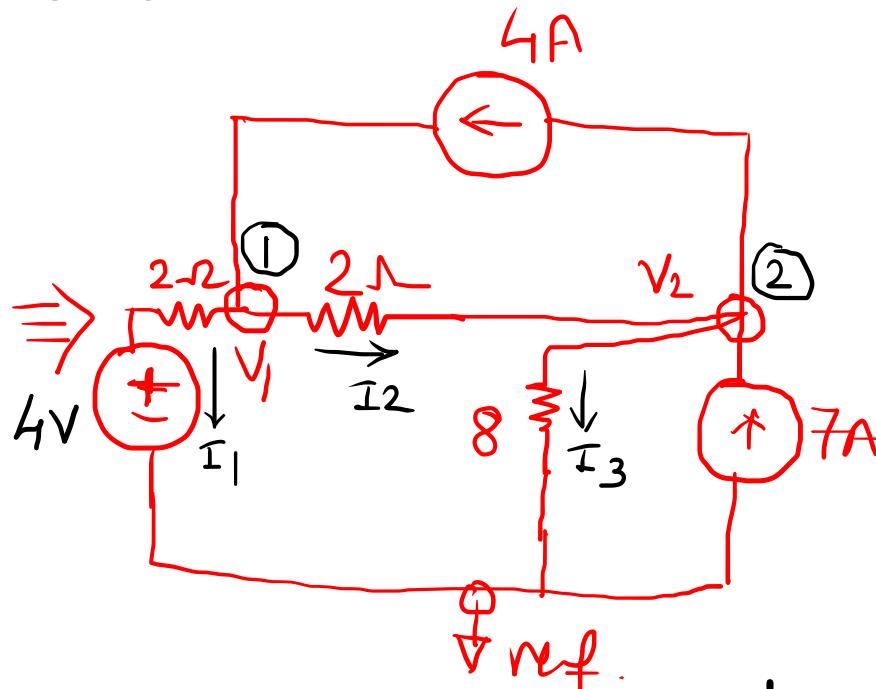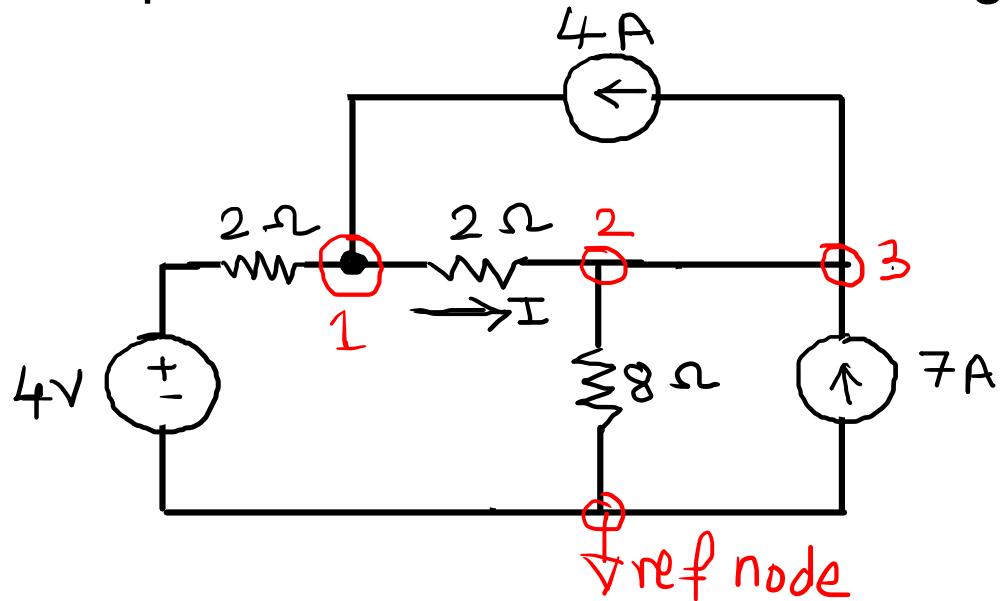Example:- 1. Find current I in following network.



Apply KCL at node ①

$$I_1 + I_2 = 4$$

$$\frac{V_1 - 4}{2} + \frac{V_1 - V_2}{2} = 4$$

$$2V_1 - V_2 = 12 \quad \text{--- } ①$$

$$\text{Solving } ① \text{ & } ② \quad V_1 = 14V \quad \text{ & } V_2 = 16V$$

KCL at node ②

$$I_2 + 7 = I_3 + 4$$

$$I_2 - I_3 = -3$$

$$\frac{V_1 - V_2}{2} - \left(\frac{V_2}{8} \right) = -3$$

$$4V_1 - 5V_2 = -24 \quad \text{--- } ②$$

$$I = \frac{V_1 - V_2}{2}$$



$$I = \frac{14 - 16}{2}$$

$$I = -1A$$

Network Analysis using nodal analysis

-1

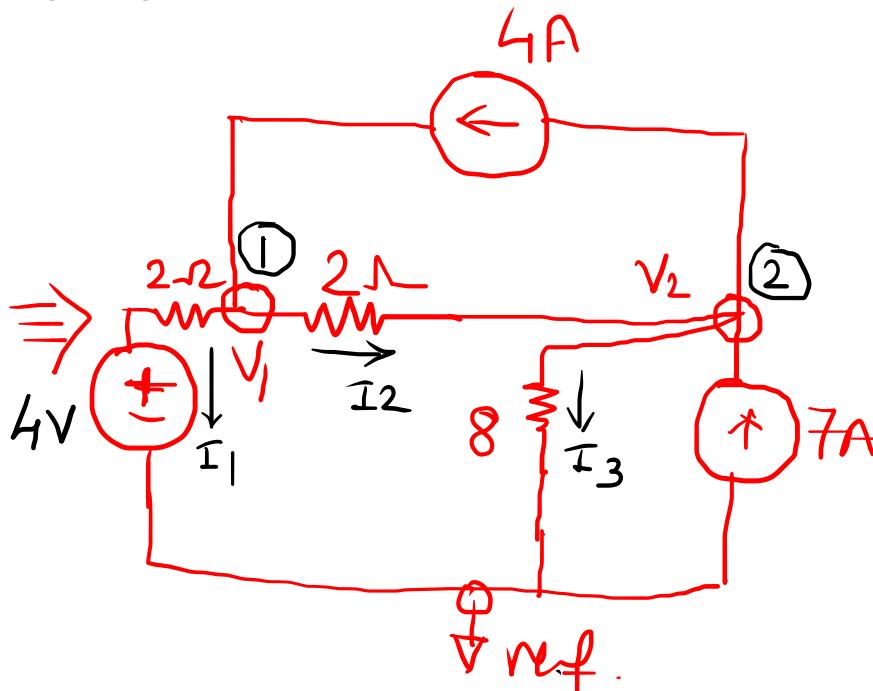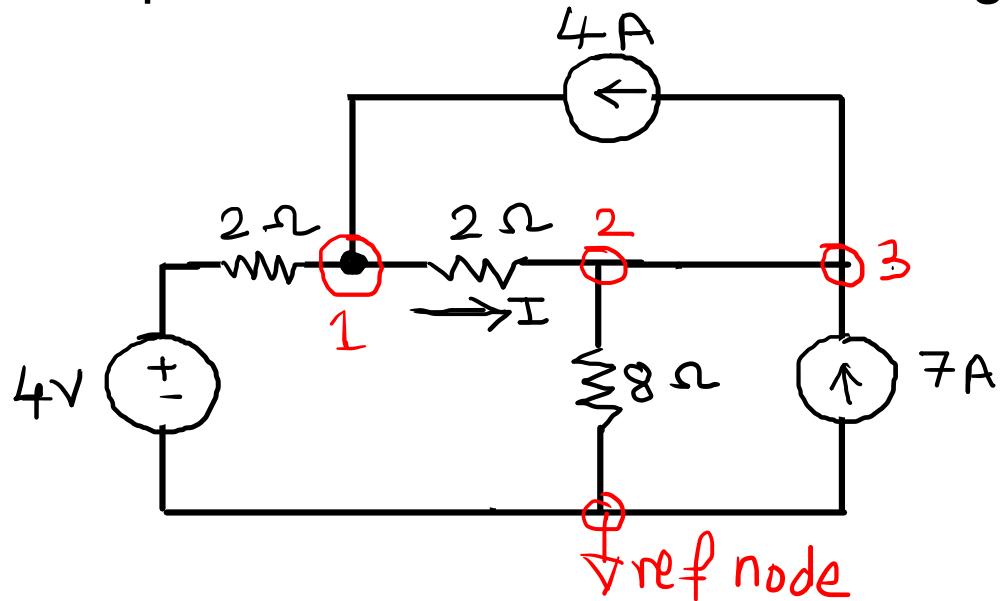Example:- 1. Find current I in following network.



→ Apply KCL at node ①

$$I_1 + I_2 = 4$$

$$\frac{V_1 - 4}{2} + \frac{V_1 - V_2}{2} = 4$$

$$2V_1 - V_2 = 12 \quad \text{--- } ①$$

→ KCL at node ②

$$I_2 + 7 = I_3 + 4$$

$$I_2 - I_3 = -3$$

$$\frac{V_1 - V_2}{2} - \left(\frac{V_2}{8} \right) = -3$$

$$4V_1 - 5V_2 = -24 \quad \text{--- } ②$$


Solving ① & ② $V_1 = 14V$ & $V_2 = 16V$

$$I = \frac{V_1 - V_2}{2}$$

$$I = \frac{14 - 16}{2}$$

$$I = -1A$$

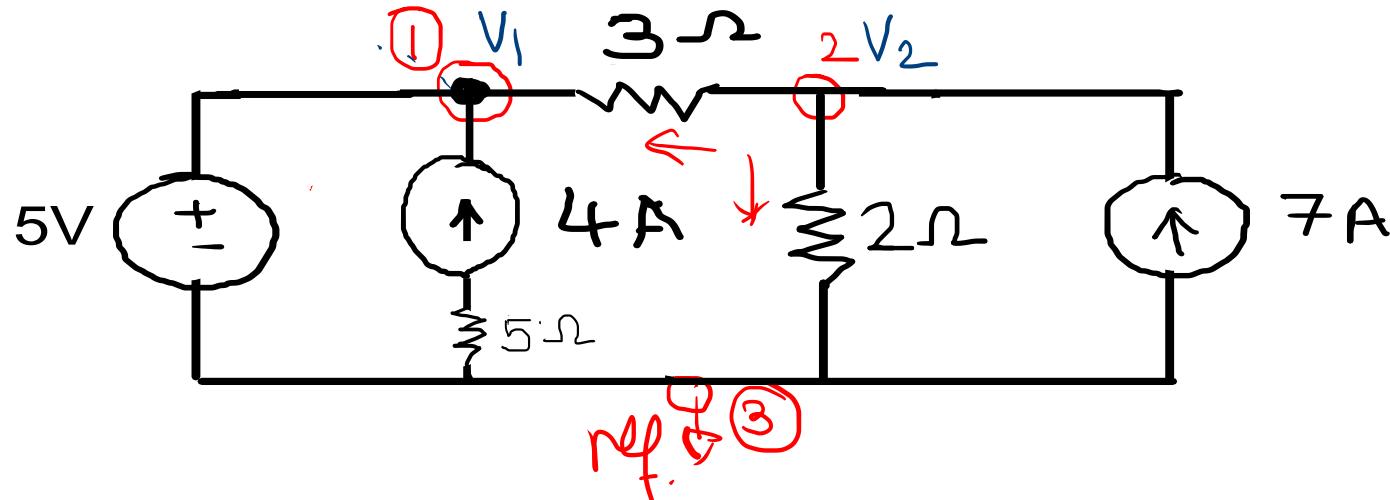Example:- 2. Find voltage across 2 Ohm resistor in the following network.



If there is a voltage source without series resistance appearing between Non-reference node and reference node then, the non-reference node voltage will be equal to value of the voltage source.

5V Source without a series resistance appeared between V₁ and Reference Node

$$V_1 = 5V$$


KCL at node ②

$$\frac{V_2 - V_1}{3} + \frac{V_2}{2} = 7 \rightarrow \text{Substitute } V_1 = 5V$$

$$V_2 = 10.4V = V_2 \text{ n.s.}$$

Network Analysis using Mesh Current Method

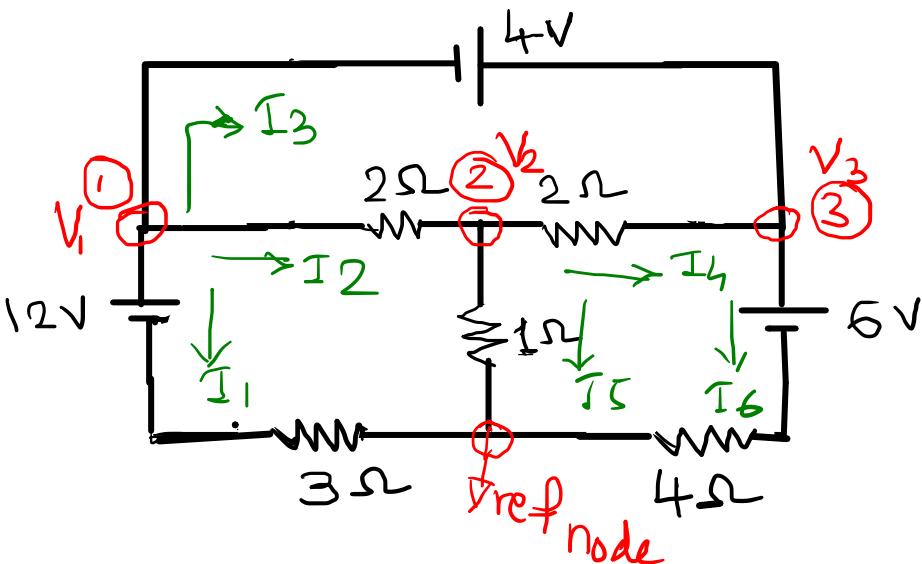Example:- 3. Find current flowing in 1 ohm resistor.



KCL at node ①

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_1 - V_2}{3} + \frac{V_1 - V_2}{2} + \frac{V_1 + 4 - V_3}{2} = 0$$

KCL at node ③

$$I_3 + I_4 = I_6$$

$$\frac{V_1 + 4 - V_3}{2} + \frac{V_2 - V_3}{2} - \frac{V_3 - 6}{4} = 0$$



KCL at node ②

$$I_2 = I_4 + I_5 \quad \checkmark$$

$$\frac{V_1 - V_2}{2} - \frac{V_2 - V_3}{2} - \frac{V_2}{1} = 0 \quad \checkmark$$

$$V_1 - 4V_2 + V_3 = 0 \quad \checkmark$$

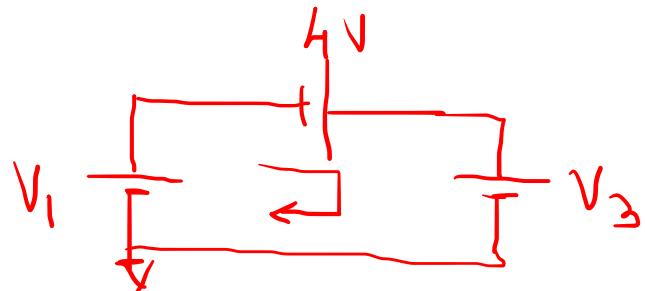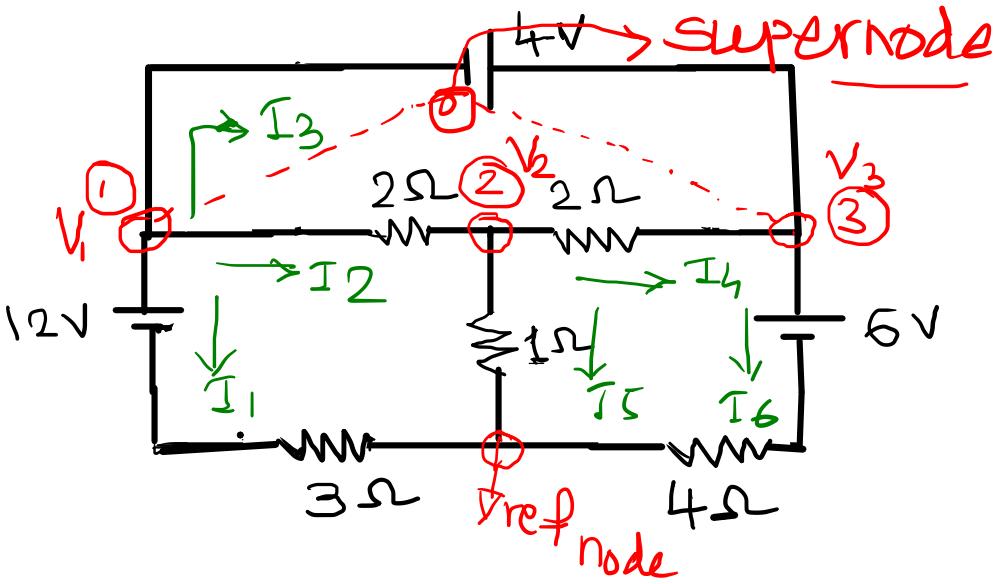If a voltage source without a series resistance appears between two non-reference nodes then write that source in terms of two non-reference node voltages (Equation-1) and form a node called supernode. Write KCL at supernode keeping non-ref node voltages intact (equation-2). We get two equations in terms of non-ref. node voltages.



Apply KVL

$$V_1 + 4 - V_3 = 0$$

$$V_1 - V_3 = -4 \quad \text{--- (1)}$$

KCL at Super node
Keep V_1 & V_3 intact to
write KCL.

$$I_1 + I_2 - I_4 + I_6 = 0$$

$$\frac{V_1 - 12}{3} + \frac{V_1 - V_2}{2} - \left(\frac{V_2 - V_3}{2} \right) + \frac{V_3 - 6}{4} = 0$$

$$\frac{4V_1 - 48 + 6V_1 - 6V_2 - 6V_2 + 6V_3 + 3V_3 - 18}{12} = 0$$


$$10V_1 - 12V_2 + 9V_3 = 66 \quad \text{--- (2)}$$

Solving (1) (2) & (3)

$$V_1 = 3.2V \quad V_2 = 2.6V \quad V_3 = 7.23V$$

$$I_{12} = \frac{V_2}{1} = 2.6A$$

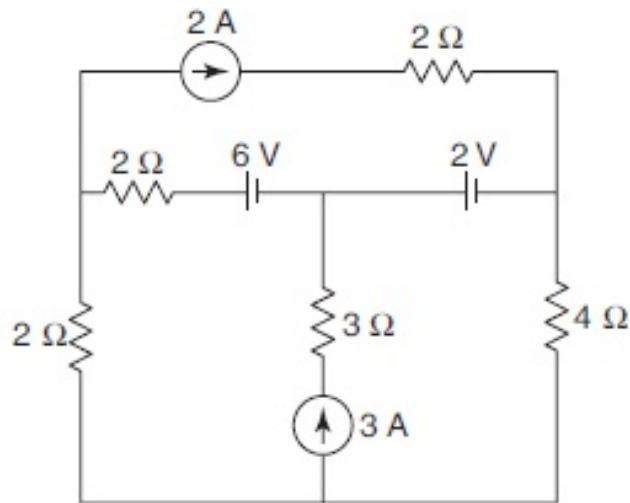Example:- 4. Find current flowing in 4 ohm resistor.



Since 2V source without series resistance b/w node ② & ③, so it's a case of supernode.

$$\therefore V_2 - 2 - V_3 = 0$$

$$V_2 - V_3 = 2 \quad \dots \textcircled{1}$$


KCL at Supernode

$$\frac{V_2 + 6 - V_1}{2} - 3 + \frac{V_3}{4} - 2 = 0$$


$$\frac{V_2 + 6 - V_1}{2} + \frac{V_3}{4} = 5$$

$$2V_2 + 12 - 2V_1 + V_3 = 20$$
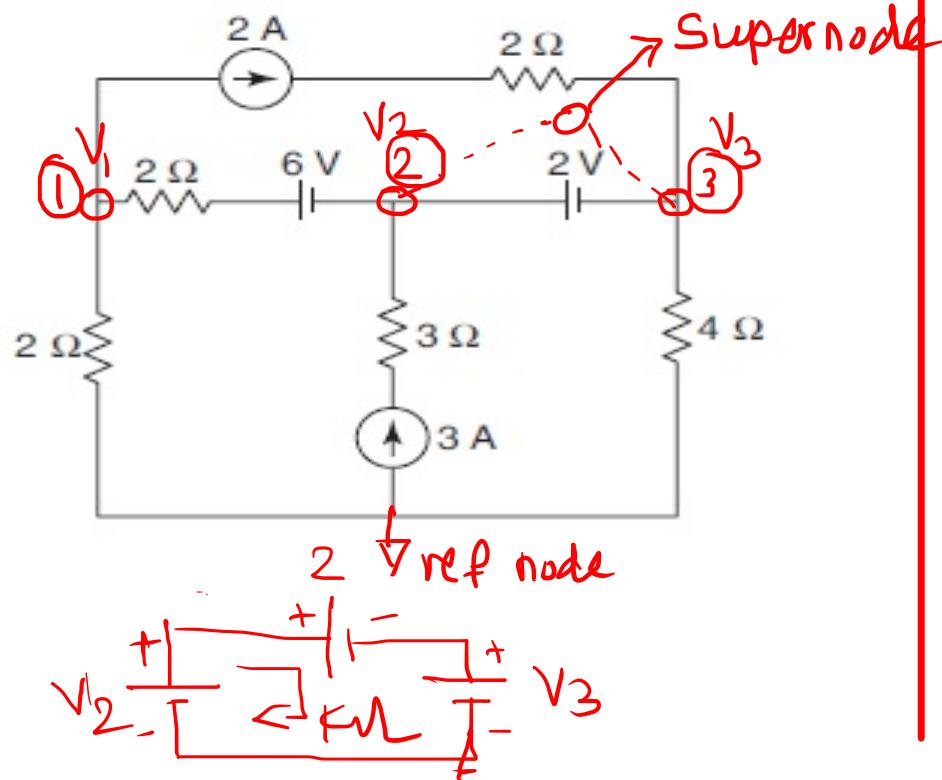
$$-2V_1 + 2V_2 + V_3 = 8 \quad \textcircled{11}$$



Example:- 4...

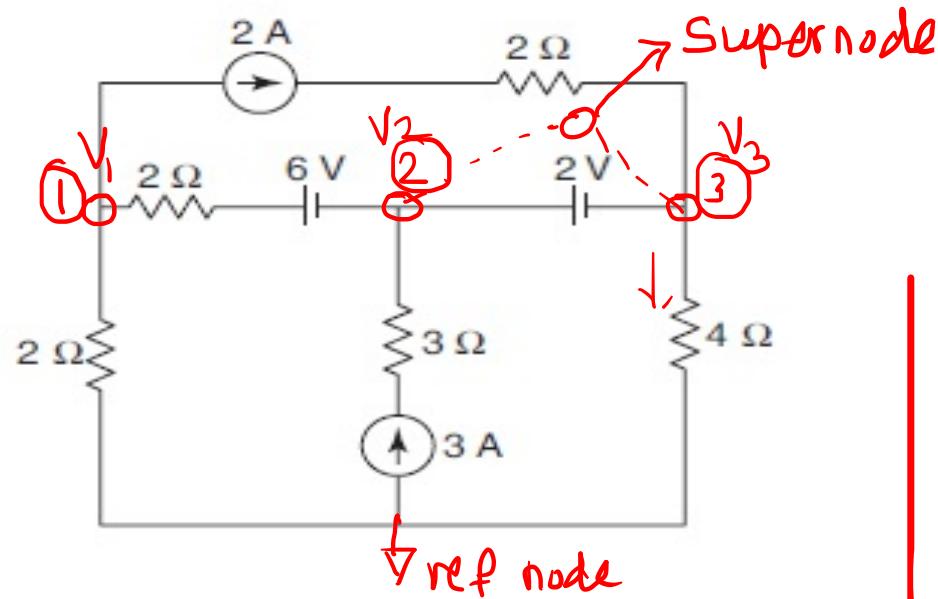

KCL at node ①

$$\frac{V_1}{2} + \frac{V_1 - 6 - V_2}{2} + 2 = 0$$

$$V_1 + V_1 - 6 - V_2 = -4$$

$$2V_1 - V_2 = 2 \quad \text{--- (III)}$$



Solving ① ② & ③

$$V_1 = 4V, V_2 = 6V, V_3 = 4V$$

$$I_{4\rightarrow 2} = \frac{V_3}{4} = \frac{4}{4} = 1A$$

Network Analysis using Mesh Current Method

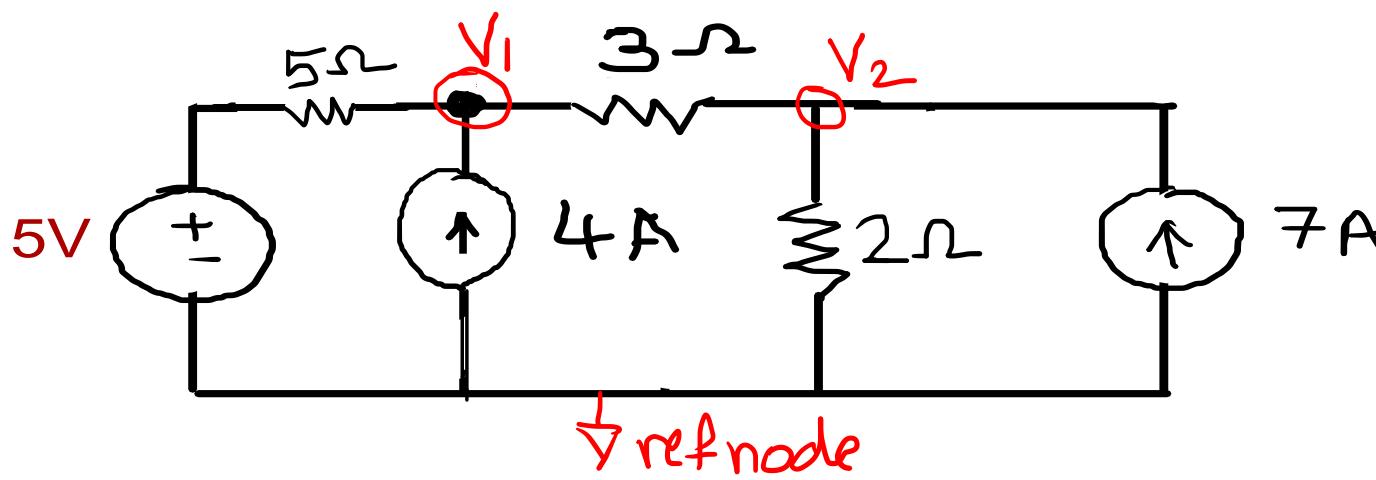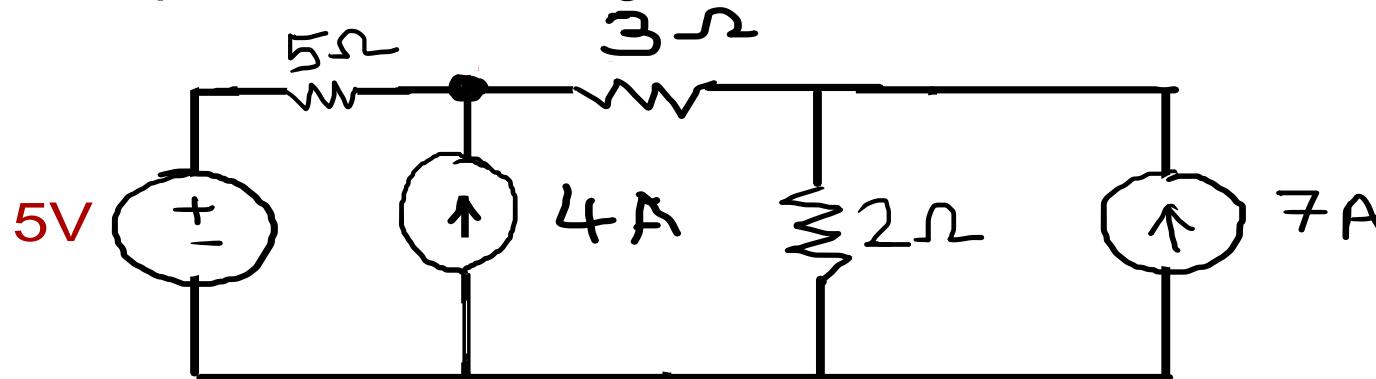Example:- 5. Find voltage across 2 Ohm resistor in the flowing network.



KCL at node ①

$$\frac{V_1 - 5}{5} + \frac{V_1 - V_2}{3} = 4$$

$$\left. \begin{aligned} \frac{3V_1 - 15 + 5V_1 - 5V_2}{15} &= 4 \\ 8V_1 - 5V_2 &= 75 \end{aligned} \right\} \quad \text{①}$$

KCL node ②

$$\frac{V_2 - V_1}{3} + \frac{V_2}{2} = 7$$

$$2V_2 - 2V_1 + 3V_2 = 42$$



$$-2V_1 + 5V_2 = 42 \quad \text{②}$$

Solving ① + ②

$$V_1 = 19.5V, V_2 = 16.2V$$

$$V_{2\Omega} = V_2 = 16.2V$$

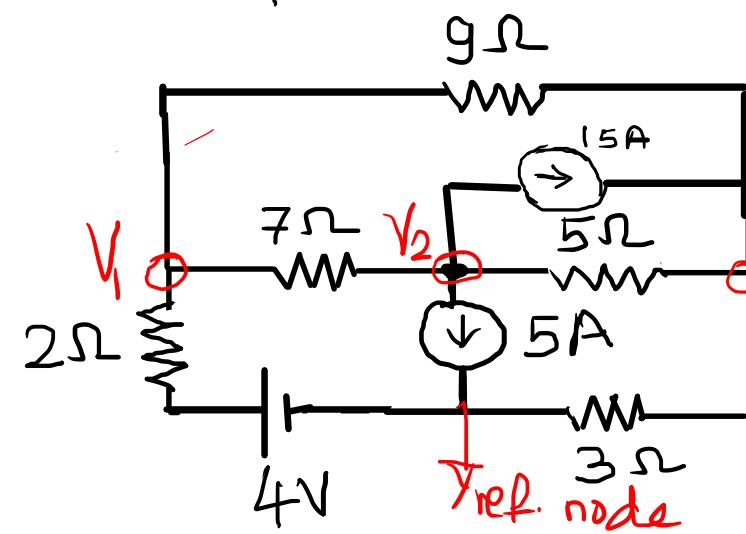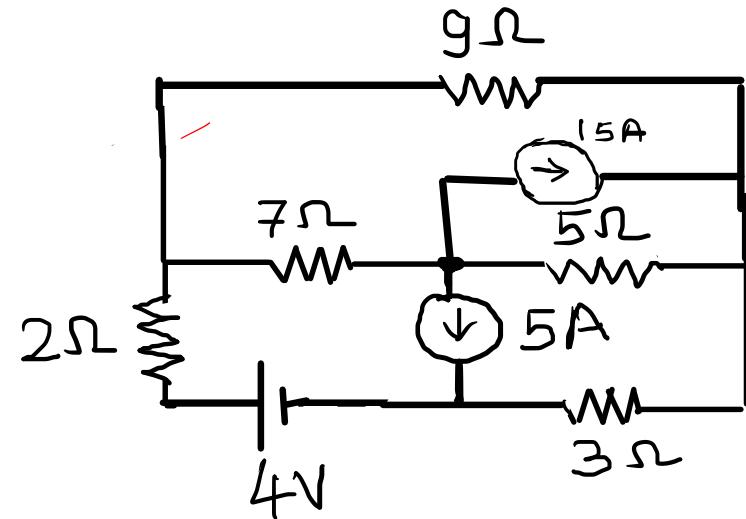Example:- 6. Find current through 3 Ohm resistor in the following network.



→ KCL at node ①

$$\frac{V_1 - 4}{2} + \frac{V_1 - V_2}{7} + \frac{V_1 - V_3}{9} = 0$$

$$95V_1 - 18V_2 - 14V_3 = 252 \quad \text{--- } ①$$

→ KCL at node ②

$$\frac{V_2 - V_1}{7} + \frac{V_2 - V_3}{5} = -20$$

$$-5V_1 + 12V_2 - 7V_3 = -700 \quad \text{--- } ②$$

→ KCL at node ③

$$\frac{V_3 - V_1}{9} + \frac{V_3 - V_2}{5} + \frac{V_3}{3} = 15$$

$$-5V_1 - 9V_2 + 29V_3 = 675 \quad \text{--- } ③$$

Solving ①, ② & ③

$$V_1 = -8.19V, V_2 = -59.82V, V_3 = 3.29V, I_{3\Omega} = \frac{V_3}{3} = 1.09A$$